

# Low Frequency LC Oscillator Hartley

