

OpAmp Inverting 3Transistor alt2

Build an op amp with three discrete transistors

