
## Oteled I ivi receiver using LA 1200 and LASSO i

FM receiver circuit redesign is the result of the Kit-Kit oft-sold in the market with IC LA1260 and LA3361 datasheets, so I think it produces better stereo sound ...

## THIS is the circuit ...

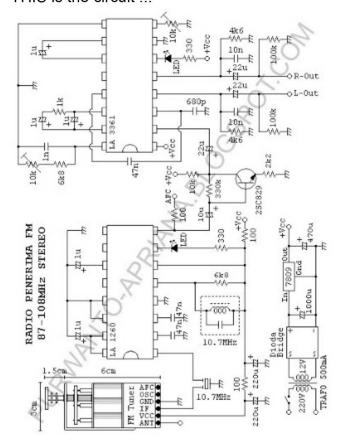

## After everything is assembled to PCB



1 of 1 24.03.2017 06:54