> IC1 LM386N

C4 100μF

SPKR1

SPEAKER

fritzing

Although I didn't build on a breadboard, this is what it could look like (stray capacitance may make this difficult):

R2 10kΩ