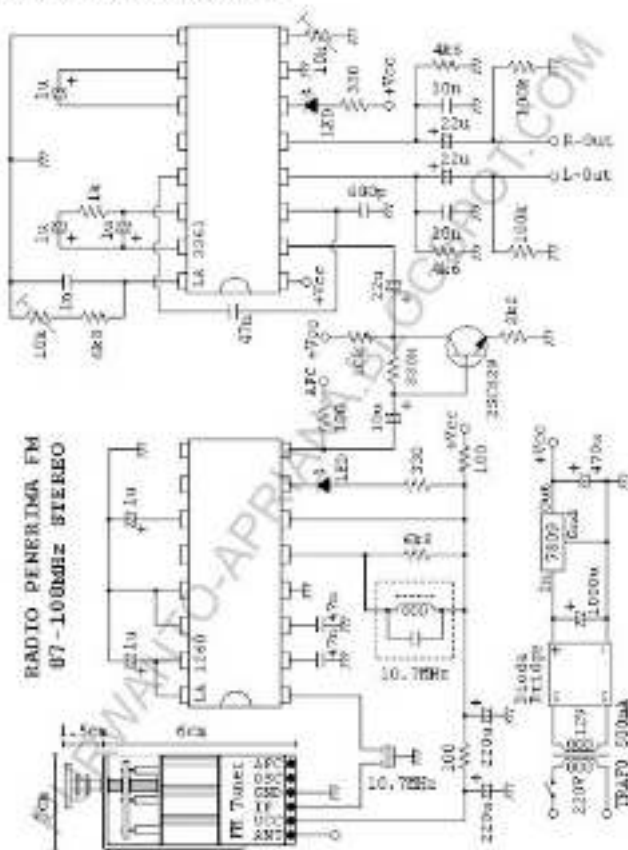


புதிதில் உருவாகிய கலாச்சாரம்

FM receiver circuit redesign is the result of the KIL-KIL off-sold in the market with IC LA1260 and LA3381 datasheets, so I think it produces better stereo sound ...

THIS is the circuit ...



After everything is assembled to PCB

