

Forced quenching improves three-transistor FM tuner

