

Triple Waveform Generator with 8038

Inside: Varius Circuits
Oscillator Circuits

The Tri-Waveform Generator can be used for a number of different uses. The one that I use it for is a signal generator to test circuits. The frequency range is 20 to 20khz. and can be adjusted by R1. The duty cycle or the time that the waveform is high and the time that the waveform is low can be adjusted by R4. The purpose of R2 and R3 are to clean up any distortion on the sine wave output. To do this you must hook up the sine wave output to an oscilloscope and adjust R2 & R3 to make the sine wave as accurate as possible.

