

# OpAmp Inverting 3Transistor alt3

Build an op amp with three discrete transistors

