
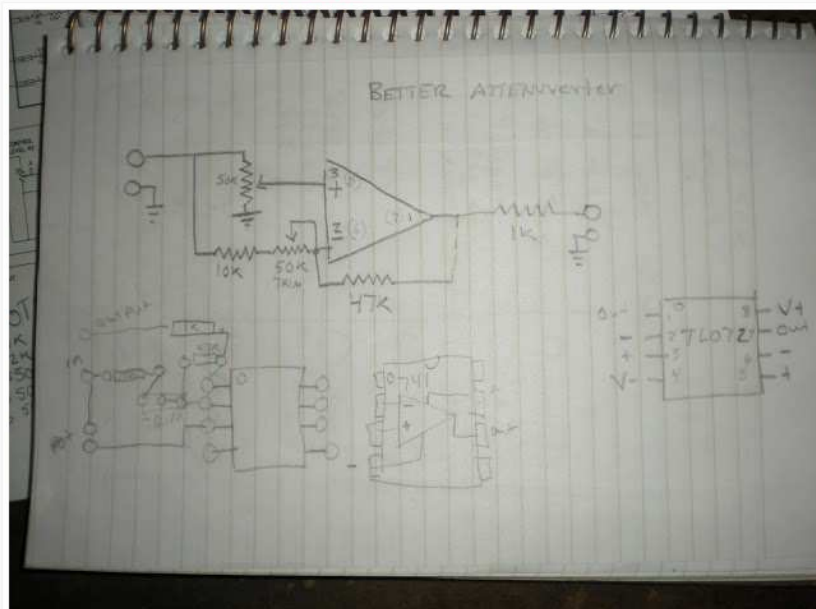


You can find these chips for like \$20 on ebay and I thought that was a minimal investment for a fun project. I ordered one and some other parts. Like all projects, I breadboarded it first to make sure it worked. I had a hard time finding a tempco 1k PTC thermistor. All I could find was NTC thermistors, so I used one of those. That was probably a mistake. I finally found some PTC 1k thermistors which I ordered today. When they come, I will replace the NTC.

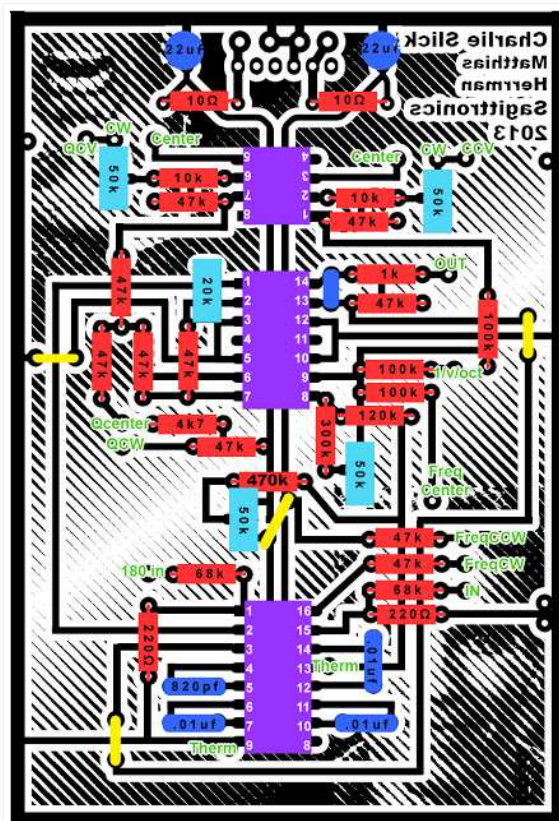



I designed a PCB for the whole project, which you are welcome to use, or you can use the one on [Fonitronik](http://fonitronik.com)



Alright, lets go over some of these labels.

TOP LEFT

QCV: resonance attenuverter input

CW: resonance attenuverter clockwise pot pin

Center: resonance attenuverter center pot pin (the CCW pin is grounded)

TOP RIGHT

CCV: cutoff attenuverter input

CW cutoff attenuverter lockwise pot pin

Center: cutoff attenuverter center pot pin (CCW pin is grounded)

ALL THE REST

OUT: filter ouput

Qcenter: Resonance pot center

QCW: resonance pot clockwise pin (CCW pin is grounded)

180 in: inverted input

1v/oct: 1 volt per octave input


Freq center: Cutoff pot center pin


Freq CCW: Cutoff pot counter clockwise pin

FreqCW: cutoff pot clockwise pin

In: regular input (CW pin of input attenuation knob, CCW to ground)




Therm: 2 points to connect thermistor



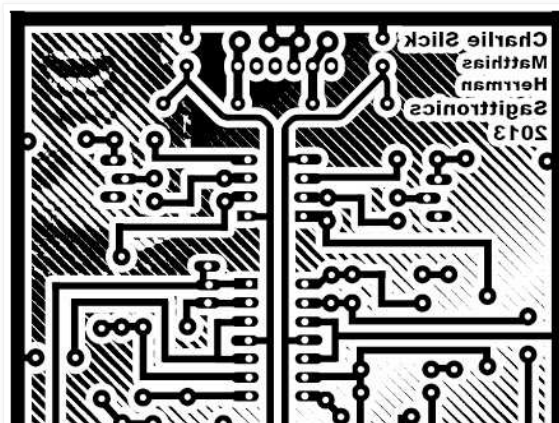


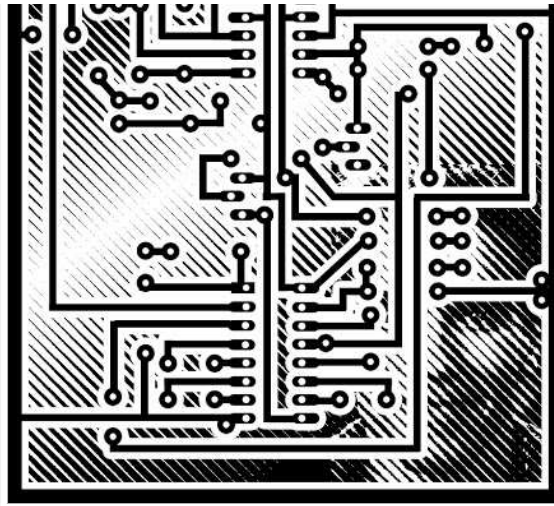


Setting the trim pots can be tricky. you need a duel channel oscilloscope to set the trim for the attenuverters. connect a sine wave or triangle wave to the attenuverter input. connect one channel of the scope to the same signal. clip the leads to the other channel on ground and pin 7 of the TL072 for resonance, then pin 1 for cut off. adjust the trim pots so that the inverted signal is equal in amplitude to the source signal. I would consult [Fonitronik](#) or the rest.

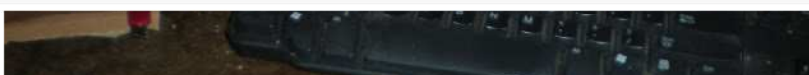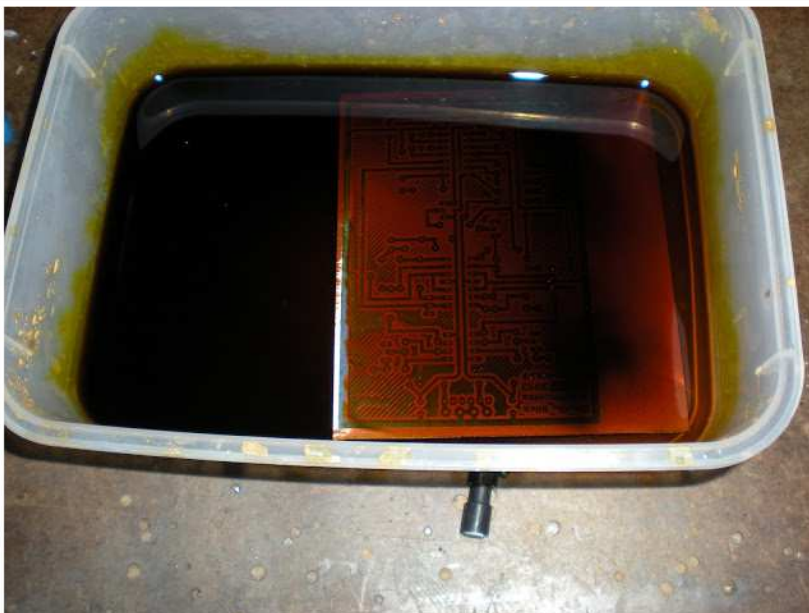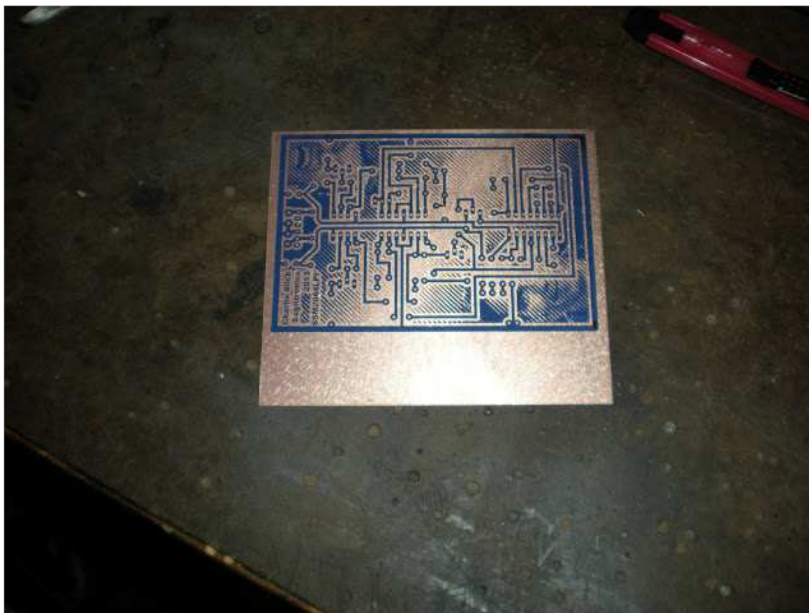
Here's some pictures of etching and assembly. The transfer turned out really good.




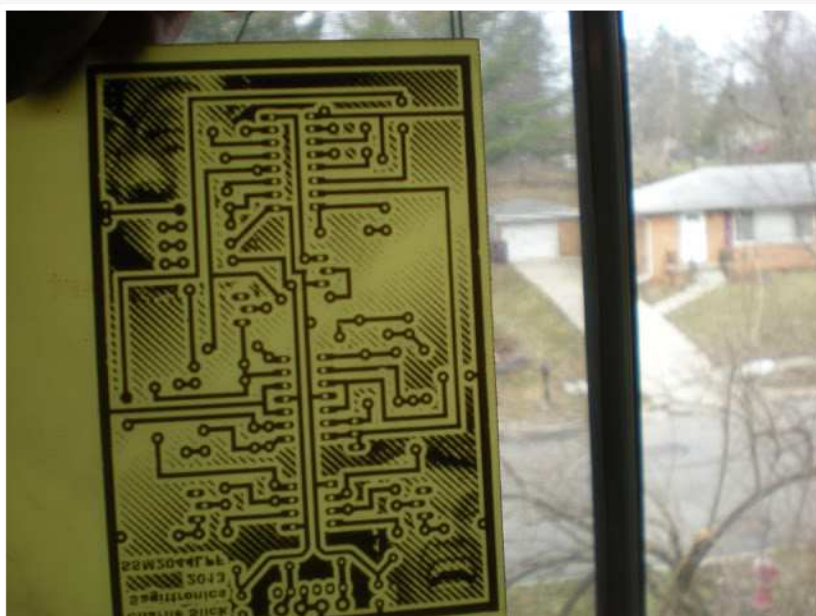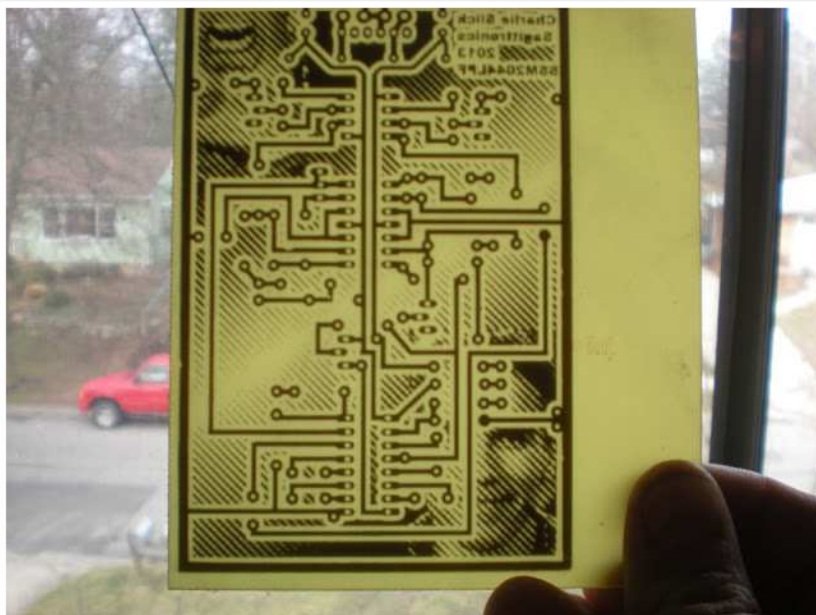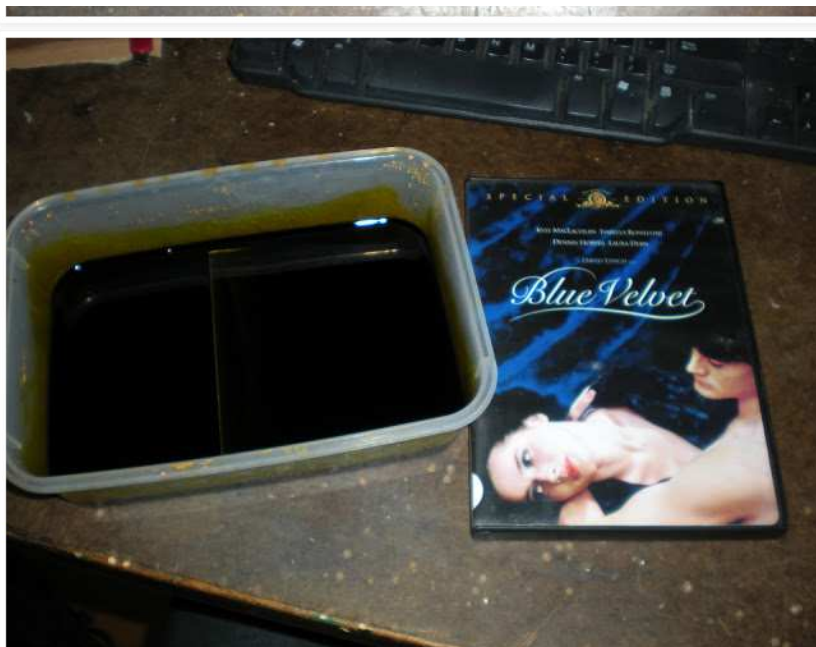

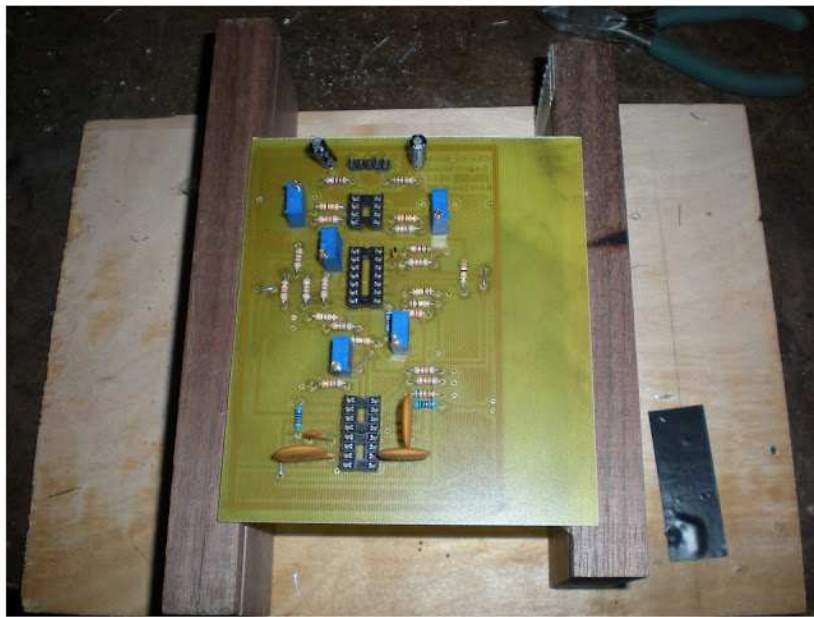

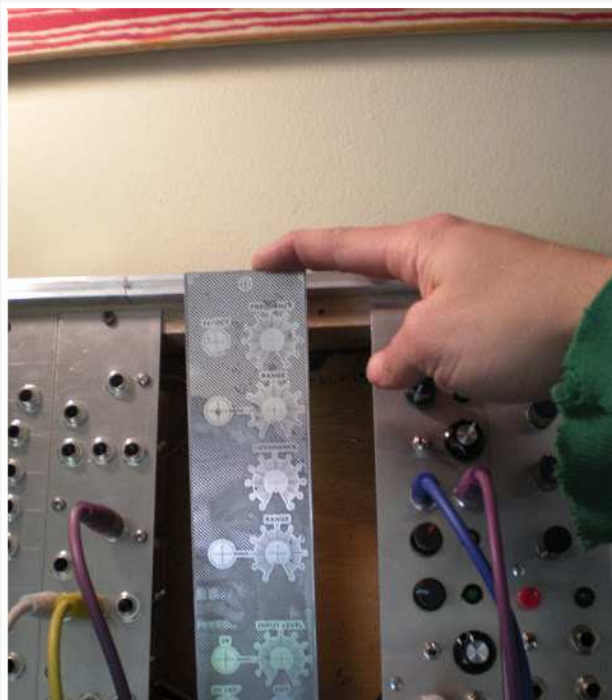As you may have seen in other posts, I've started etching my aluminum front panels. This project has been Total Recall themed.



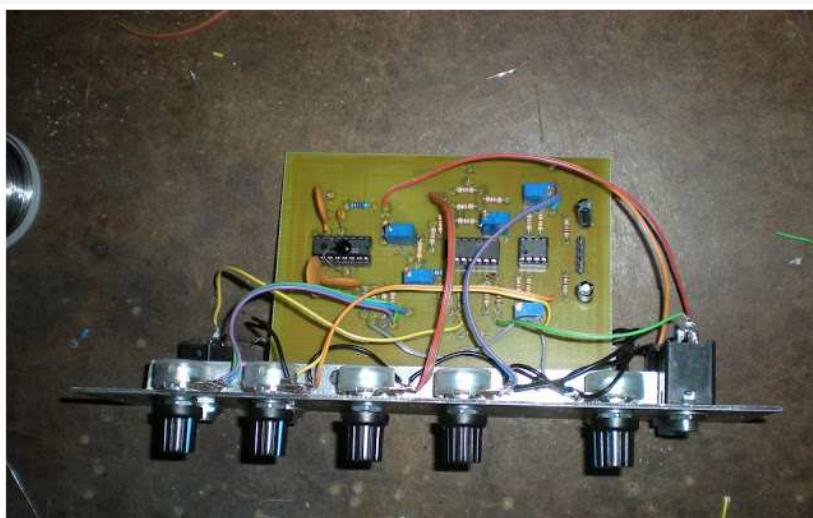



and finally a video. enjoy.

...

Posted by [Charlie](#) at [8:48 PM](#)

Labels: [2044](#), [etch.](#), [filter](#), [korg](#), [low pass](#), [LPF](#), [mono](#), [monopoly](#), [pcb](#), [poly](#), [schematic](#), [ssm2044](#)

1 comment :



Meghana Naidu October 8, 2014 at 12:58 AM

Its a nice blog posted by you. I was looking for this type of blog that is fresh and interesting articles. thank you...!
[Chip Level Training in Hyderabad](#)