

# Low Frequency LC Oscillator

